

Finals Physics Review Practice Answer

MCQ

1. C
2. D
3. D
4. D
5. D
6. D
7. C
8. D
9. A
10. A
11. B
12. A
13. C
14. D
15. C
16. D


True and False

1. True
The right-hand rule relates current direction to the magnetic field in a solenoid.
2. True
3. False
4. False

Calculation

- 1.
2. 1.4×10^{-6} T into the page B is 3% of BE
3. near: 4.4×10^{-2} N/m attractive

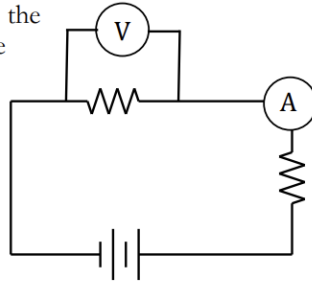a. The voltmeter must be placed *over* the resistor to measure the potential difference before and after.



b. The ammeter must be inserted *into* the circuit so that there is only one path for current to follow. The ammeter may be placed anywhere in the circuit to measure current because it's a series circuit and the current is the same everywhere. But it makes most sense intuitively to place the meter near the resistor.

- c. The two resistors are in series, so the current I is the same throughout the circuit. Using Ohm's Law and the information we have for R_1 :

$$V_1 = IR_1$$

$$3V = (0.005A)R_1$$

$$R_1 = \frac{3}{0.005} = 600\Omega$$

- d. Using the stated current and resistance:

$$P = I^2 R$$

$$P = (0.005A)^2 (1000\Omega) = 2.5 \times 10^{-2} W = 25mW$$

- e. The terminal voltage of the battery can be calculated using the total I and R for the circuit, along with Ohm's Law:

$$V = IR$$

$$V = (0.005A)(600\Omega + 1000\Omega) = 8.00V$$

- f. Terminal voltage is emf less the potential drop due to the internal resistance:

$$V = \mathcal{E} - Ir$$

$$8 = 8.2 - (0.005)r$$

$$r = 40\Omega$$

far: 2.2×10^{-2} N/m repulsive